



Welcome to The Logic Design Lab!

Fall 2019 Lab 3: Sequential Circuits

Prof. Chun-Yi Lee

Department of Computer Science
National Tsing Hua University

Agenda

- Lab 3 Outline
- Lab 3 Basic Questions
- Lab 3 Advanced Questions



Lab 3 Outline

- Basic questions (1.5%)
 - Individual assignment
 - Due on **10/17/2019. In class.**
 - Only demonstration is necessary. Nothing to submit.
- Advanced questions (5%)
 - Group assignment
 - ILMS submission due on **10/17/2019. 23:59:59.**
 - Demonstration on your FPGA board (**In class**)
 - Assignment submission (**Submit to ILMS**)
 - Source codes and testbenches
 - Lab report in PDF

Lab 3 Rules

- Please note that grading will be based on **NCVerilog**
- You can use **ANY** modeling techniques
- If not specifically mentioned, we assume the following SPEC
 - **CLK** is **positive edge triggered**
 - Synchronously reset the Flip-Flops when **RESET == 1'b0**

Lab 3 Submission Requirements

- Source codes and testbenches
 - Please follow the templates **EXACTLY**
 - We will test your codes by TAs' testbenches
- Lab 3 report
 - Please submit your report in a single **PDF** file
 - Please **draw** the block diagrams of your designs by **yourself**
 - Please **explain** your designs in detail
 - Please **list** the contributions of each team member clearly
 - **Please explain how you test your design**
 - What you have **learned** from Lab 3

Agenda

- Lab 3 Outline
- **Lab 3 Basic Questions**
- Lab 3 Advanced Questions





Basic Questions

- Individual assignment
- Verilog questions (due on 10/17/2019. In class.)
 - Clock Divider
 - 4-bit Ping-Pong Counter
- Demonstrate your work by waveforms



Verilog Question 1

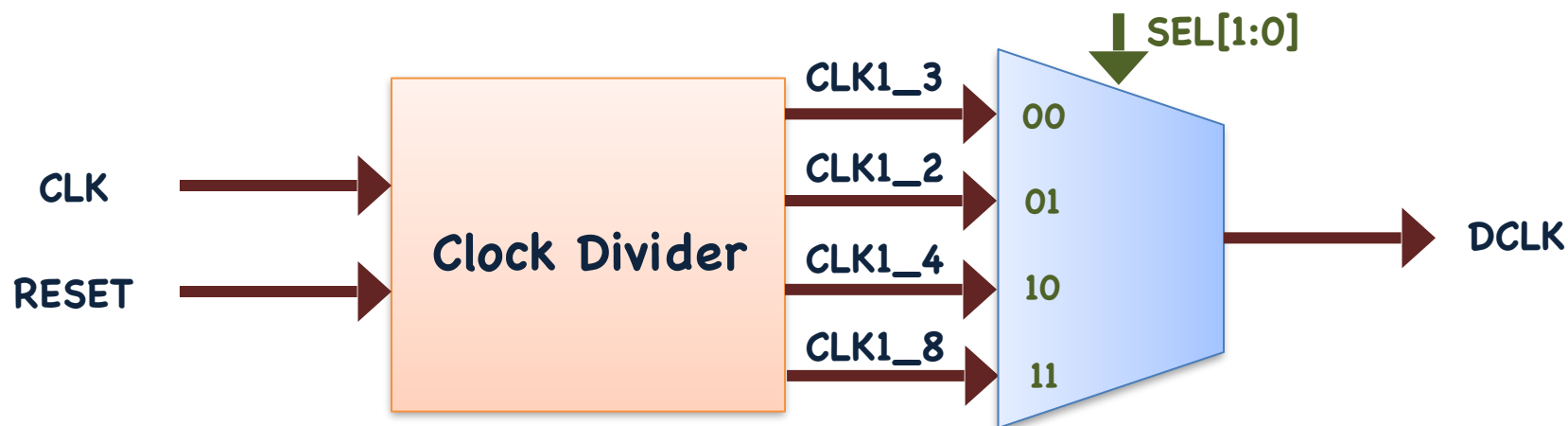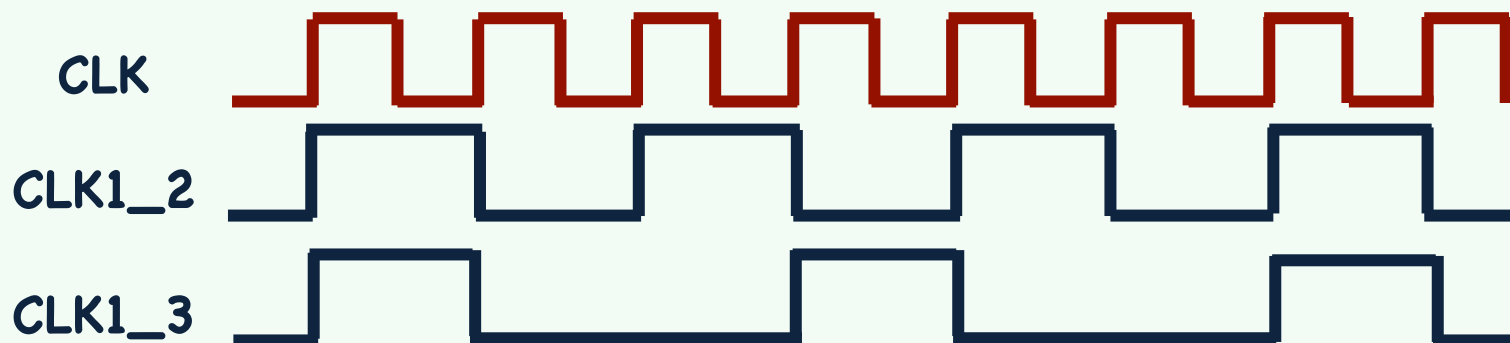- Clock Divider
 - SEL[1:0] and the mux are combinational, not triggered by CLK
 - **Outputs: CLK1_2, CLK1_4, CLK1_8, CLK1_3, DCLK**



Verilog Question 1(Con't)

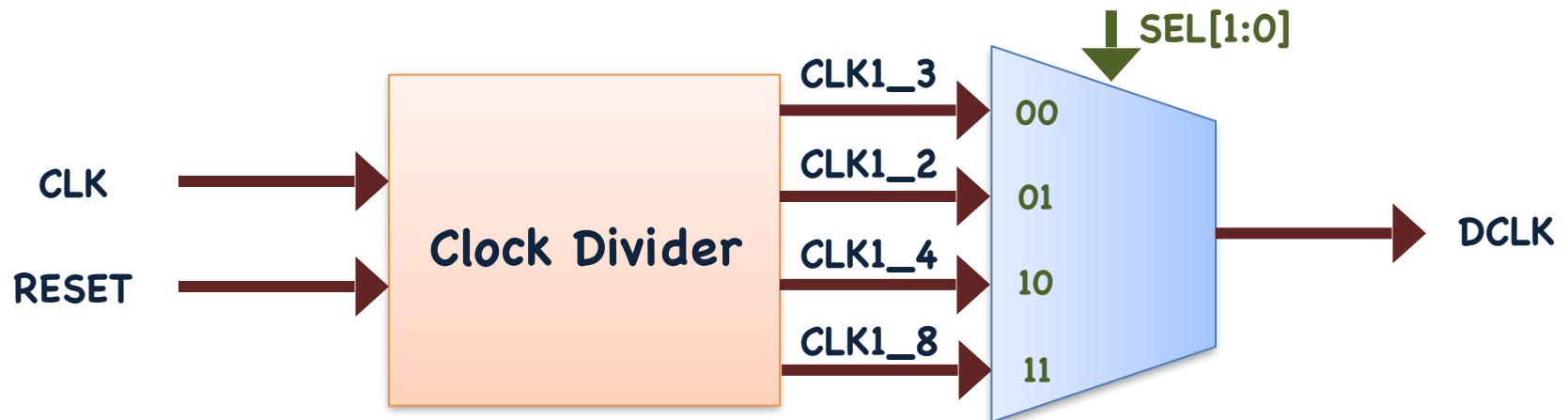 - Clock Divider
 - SEL[1:0] and the mux are combinational, not triggered by CLK
 - **Outputs: CLK1_2, CLK1_4, CLK1_8, CLK1_3, DCLK**




Verilog Question 2

- Design a 4-bit Ping-Pong Counter
 - Out: 0,1,2,...,13,14,15,14,13,...,2,1,0,1,2,...
 - Direction: 0,0,0,...,0, 0, 0, 1, 1,..., 1,1,1,0,0,...
- SPEC
 - When **RESET** == 1'b0, the counter resets its value to 4'b0000
 - When **Enable** == 1'b1, the counter begins its operation.
Otherwise, the counter holds its current value



Agenda

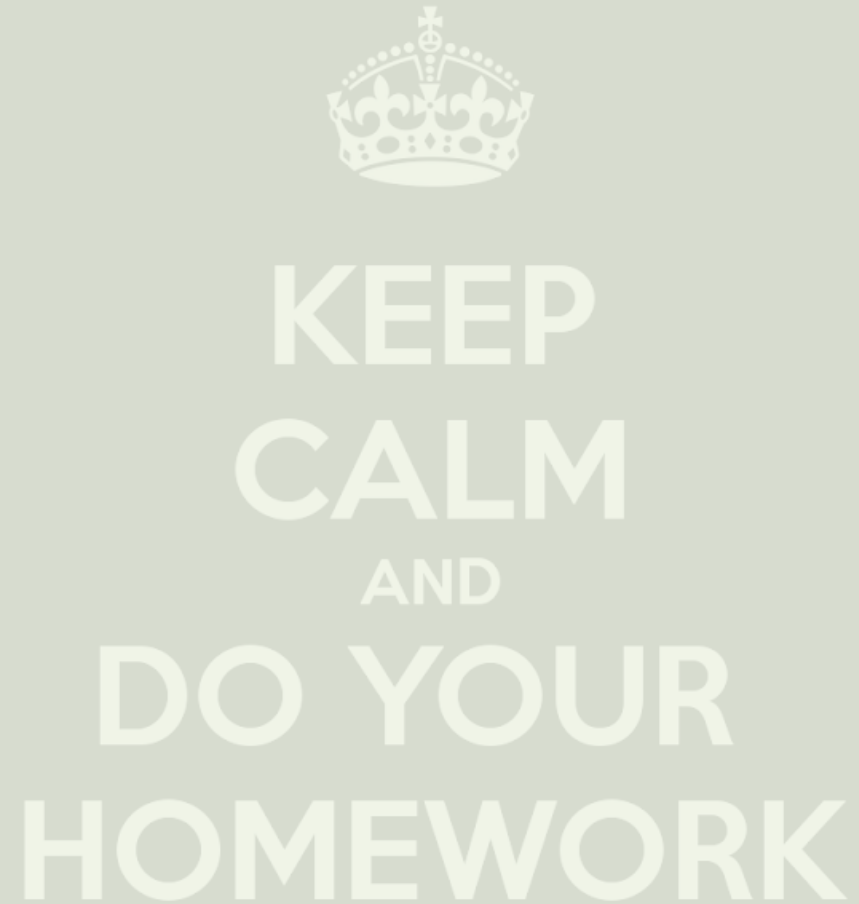- Lab 3 Outline
- Lab 3 Basic Questions
- **Lab 3 Advanced Questions**




Advanced Questions

- Group assignment
- Verilog questions (due on 10/17/2019. 23:59:59.)
 - Linear-Feedback Shift Register
 - 64 x 8 memory array
 - 4-bit Paramterized Ping-Pong Counter
- FPGA demonstration (due on 10/17/2019. In class.)
 - 4-bit Paramterized Ping-Pong Counter on FPGA

Verilog Question 1

- Linear-Feedback Shift Register (LFSR)

 

- When **RESET == 1'b0**, reset DFF[4:0] to **5'b01000**
- Please draw the **state transition diagram** of the DFFs in LFSR
- Please describe what happens if we reset the DFFs to **5'b00000**


Verilog Question 2

- 64 x 8 memory array **MEM**
 - **M** = 64, **N** = 8
 - **Inputs:** CLK, REN, WEN, ADDR[5:0], DIN[7:0]
 - **Outputs:** DOUT[7:0]



Verilog Question 2 Specification

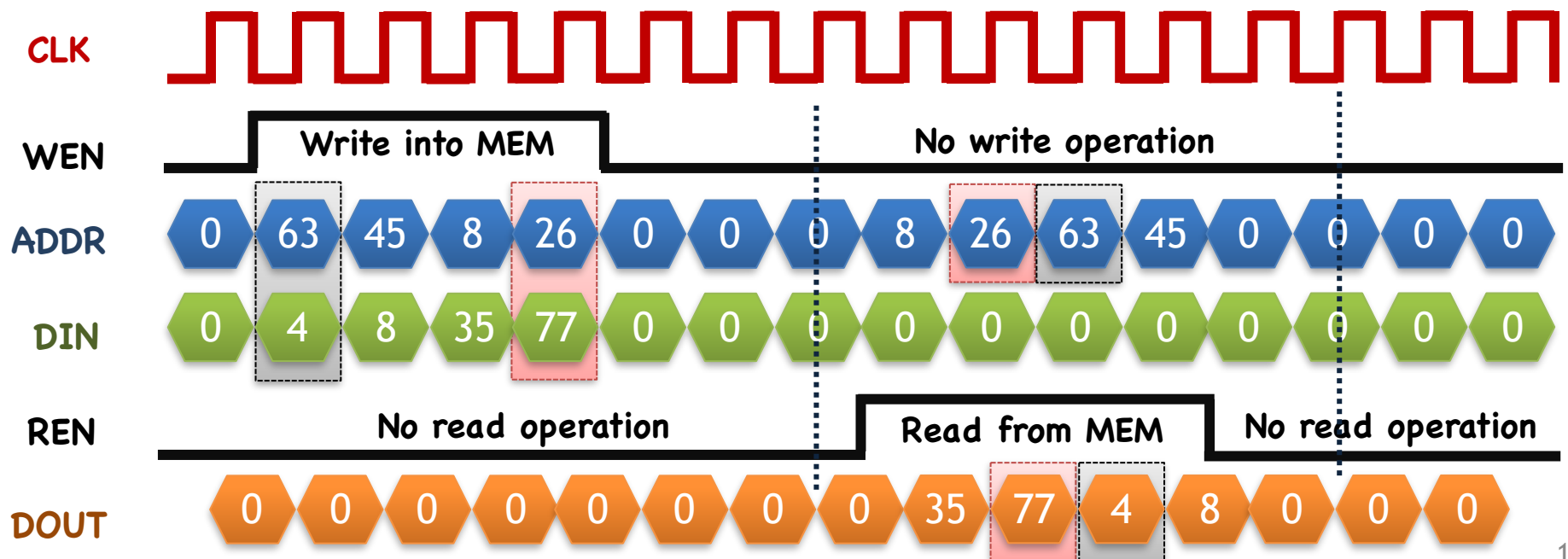- Specification
 - When $WEN == 1'b1$, write DIN to $MEM[ADDR]$
 - When $REN == 1'b1$, output $MEM[ADDR]$ to $DOUT$; otherwise $DOUT = 8'd0$
 - REN and WEN won't be one at the same time. **If both are 1, do only the read operation**
 - **MEM** does not need to be reset



Verilog Question 3

- Design a **4-bit Ping-Pong Counter** with **MAX** and **MIN**
 - Input: **CLK, RESET, Enable, FLIP, MAX[3:0], MIN[3:0]**
 - Out: **0,1,2,...,7,8,9,8,7,...,2,1,0,1,2,...**
 - Direction: **0,0,0,...,0,0,0,1,1,...,1,1,1,0,0,...**
 - In the above example, **MAX** is 9 and **MIN** is 0



Verilog Question 3 Specification

■ 4-bit Ping-Pong Counter SPEC

- When **RESET** == 1'b0, the counter resets its value to **MIN**
- When **Enable** == 1'b1, the counter begins its operation. Otherwise, the counter holds its current value

■ **MAX** and **MIN**

- **MAX** and **MIN** values are the maximum and minimum values for the counter
- **MAX** > **MIN**. Otherwise, the counter holds its current value
- When counter > **MAX** or counter < **MIN**, counter holds its current value

■ **FLIP**

- When **FLIP** == 1'b1, counter flips its direction
- Flip is **only one cycle** in length
- Flip occurs when counter < **MAX** and counter > **MIN**

Verilog Question 3 Specification

■ Notes

- Be careful that **MAX** and **MIN** will change during counting
- Once the value of the counter is out of range, hold the value and direction
- If **MAX == MIN == output**, please hold the **output** and **direction**
- You **MUST** add debounce and one-pulse circuits for your buttons
- Your counter should count in an observable frequency so that TAs can tell whether your design is correct or not

Advanced Questions

- Group assignment
- Verilog questions (due on 10/17/2019. 23:59:59.)
 - Linear-Feedback Shift Register
 - 64 x 8 memory array
 - 4-bit Paramterized Ping-Pong Counter
- **FPGA demonstration** (due on 10/17/2019. In class.)
 - 4-bit Paramterized Ping-Pong Counter on FPGA

FPGA Demonstration 1

- 4-bit Paramterized Ping-Pong Counter on FPGA
- **Behavior specification**
 - In the beginning, the digits showing on the 7-segment display should be **MIN**
 - Once **Enable** is on, the Ping-Pong Counter starts counting
 - When **Enable** is off, the Ping-Pong Counter holds its value
 - The Ping-Pong Counter only counts when **MAX > MIN**
- **Switches**
 - **SW[0]** stands for **Enable**
 - **SW[4:1]** stand for **MIN**
 - **SW[8:5]** stand for **MAX**

FPGA Demonstration 1

■ Buttons

■ "UP" button stands for Flip

- Once flip occurs, you should change your direction

- Flip only occurs when **MIN** \leq output \leq **MAX**

■ "DOWN" button stands for **RESET**

- Once the button is pushed, the output is set to **MIN**, which is determined by **SW[4:1]**

- The direction is set to "counting up"

■ Please present your output signal on the two right most 7-segment displays


FPGA Demonstration 1

■ 7-segment display


- The leftmost two digits of the 7-segment displays stand for **direction**
- Please illuminates the upper three segments when counting up, and illuminates the lower three segments otherwise
- Please see the figure on the next page for more details

FPGA Demonstration 1

Counting Up

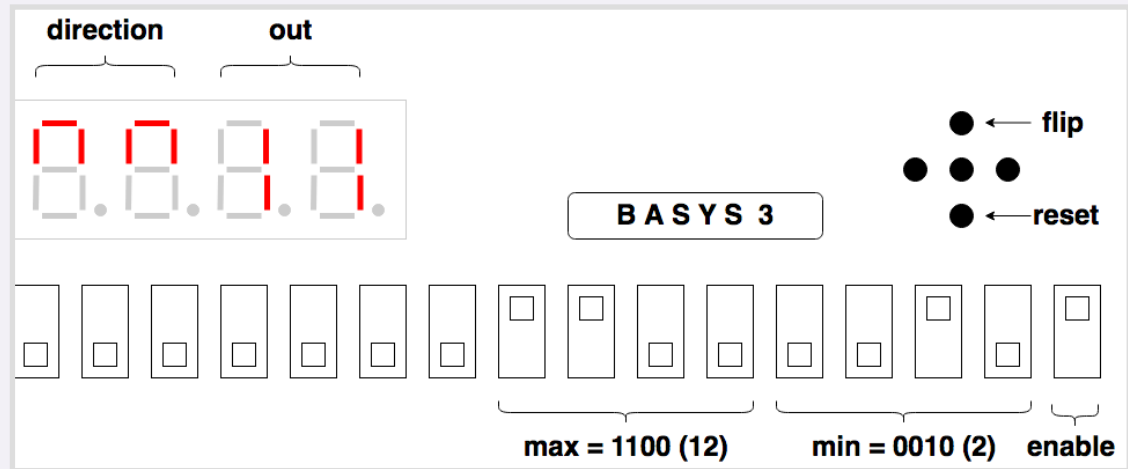

Counting Down

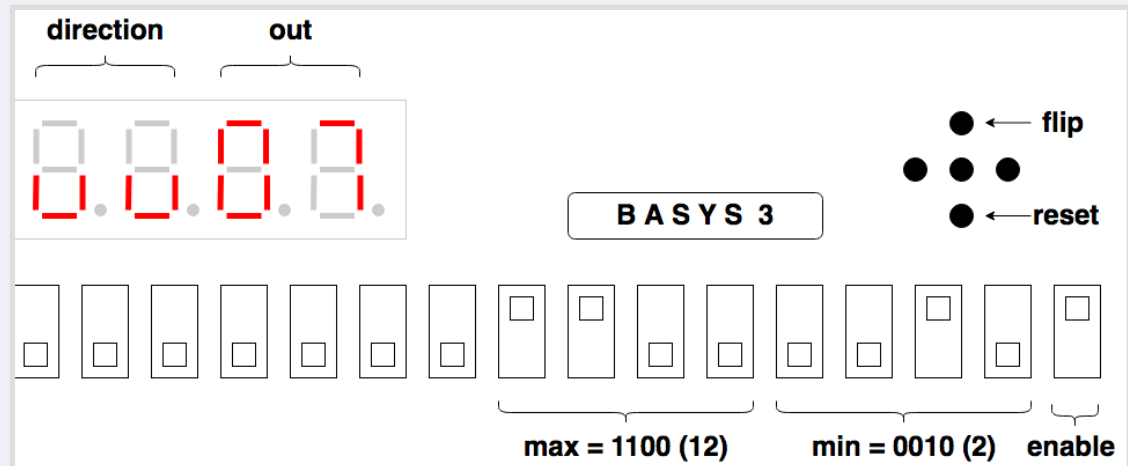

FPGA Demonstration 1

■ Notes

- Be careful that **MAX** and **MIN** will change during counting
- Once the value of the counter is out of range, hold the value and direction
- If **MAX == MIN == output**, please hold the **output** and **direction**
- You **MUST** add debounce and one-pulse circuits for your buttons
- **Remember to add debounce and one-pulse circuits to your design**
- We use the **100MHz** clock which is provided by the FPGA board. Please set **clk** as input and connect it with the **W5** port on the FPGA board.
- Your counter should count in an observable frequency so that TAs can tell whether your design is correct or not



Thank you for your attention!

*Balloon Festival at Reno, Nevada, USA
This picture is taken by Chun-Yi Lee himself, who is also a fan of photography